
```

disp('A. The circuit behaves like a low pass filter')
disp('B. I would expect that the circuit has a passband at lower
      frequency and a 2nd order drop off will happen at cut-off frequency')

clear all

runTime = 1; %seconds
timecuts = 1000;
dt =runTime/timecuts;

R1=1;
C1=0.25;
R2=2;
L1=0.2;
R3=10;
a=100;
R4=0.1;
Ro=1000;

%      V1      V2      V3      V5      IL3
% G = [-1/R1, 0,      0,      0,      0; ...%N1
%       1/R1 , -1/R2, 0,      0,      0; ...%N2
%       0,      0,      -1/R3, 0,      0; ...%N3
%       0,      0,      -a/(R3*R4), -1/R4, 0; ...%N4

C = [ 0, 0, 0, 0, 0, 0, 0; ...
      -C1,C1, 0, 0, 0, 0, 0; ...
      0, 0, -L1, 0, 0, 0, 0; ...
      0, 0, 0, 0, 0, 0, 0; ...
      0, 0, 0, 0, 0, 0, 0; ...
      0, 0, 0, 0, 0, 0, 0; ...
      0, 0, 0, 0, 0, 0, 0];

G = [ 1,      0, 0, 0, 0, 0, 0; ...
      -1/R1, (1/R2 + 1/R1), -1, 0, 0, 0, 0; ...
      0,      1, 0, -1, 0, 0, 0; ...
      0,      0, -1, 1/R3, 0, 0, 0; ...
      0,      0, 0, 0, -a, 1, 0; ...
      0,      0, 0, 1/R3, -1, 0, 0; ...
      0,      0, 0, 0, 0, -1/R4, (1/R4 + 1/Ro)];

%Time Step function
V1 = 0;
F = zeros(7,1);
Flist = zeros(7,1,timecuts);
Flist(1,1,30:timecuts) = 1;
Vlist = zeros(7,1,timecuts);

for count = 2:1:timecuts

```

```

    A = C/dt +G;

    Vlist(:, :, count) = A\((C*Vlist(:, :, count-1)/dt +Flist(:, :, count)));
end

V1list(1, :) = Vlist(1, 1, :);
V2list(1, :) = Vlist(2, 1, :);
ILlist(1, :) = Vlist(3, 1, :);
I3list(1, :) = Vlist(4, 1, :);
V4list(1, :) = Vlist(5, 1, :);
Volist(1, :) = Vlist(7, 1, :);

figure(1)
plot((1:timecuts).*dt, Volist(1, :))
xlabel('Time(s)')
ylabel('Voltage')
title('Vin and Vout of Step function')
hold on
plot((1:timecuts).*dt, V1list(1, :))
hold off

figure(2)
g = abs(fftshift(fft(Volist(1, :))));
plot(((1:length(g))/timecuts)-0.5, g)
xlim([-0.05 0.05])
xlabel('frequency')
ylabel('magnitude')
title('Fourier transform of output')

%Sine(2*pi*f*t)function with f = 1/(0.03)HZ
f = 1/0.03;
Flist = zeros(7, 1, timecuts);
for count = 1:1:timecuts
    Flist(1, 1, count) = sin(2*pi*f*count*dt);
end
Vlist = zeros(7, 1, timecuts);

for count = 2:1:timecuts
    A = C/dt +G;

    Vlist(:, :, count) = A\((C*Vlist(:, :, count-1)/dt +Flist(:, :, count)));
end

V1list(1, :) = Vlist(1, 1, :);
V2list(1, :) = Vlist(2, 1, :);
ILlist(1, :) = Vlist(3, 1, :);
I3list(1, :) = Vlist(4, 1, :);
V4list(1, :) = Vlist(5, 1, :);
Volist(1, :) = Vlist(7, 1, :);

figure(3)

```

```

plot((1:timecuts).*dt,Volist(1,:))
xlabel('Time(s)')
ylabel('Voltage')
title('Vin and Vout of Sine wave')
hold on
plot((1:timecuts).*dt,Vl1list(1,:))
hold off

figure(4)
g = abs(fftshift(fft(Volist(1,:))));
plot(((1:length(g))/timecuts)-0.5,g)
xlim([-0.05 0.05])
xlabel('frequency')
ylabel('magnitude')
title('Fourier transform of output')

%Gaussian pulse with magnitude of 1 std dev of 0.03s and delay of
0.06s
%Vgauss = exp(-1/2*((k/ts-0.06)/(0.03))^2)
mag = 1;
dev = 0.03;
delay = 0.06;
Flist = zeros(7,1,timecuts);
for count = 1:1:timecuts
    Flist(1,1,count) = exp(-((count*dt-0.06)/0.03)^2);
end
Vlist = zeros(7,1,timecuts);

for count = 2:1:timecuts
    A = C/dt +G;

    Vlist(:, :,count) = A\((C*Vlist(:, :,count-1)/dt +Flist(:, :,count)));
end

Vl1list(1,:) = Vlist(1,1,:);
Vl2list(1,:) = Vlist(2,1,:);
Vl3list(1,:) = Vlist(3,1,:);
Vl4list(1,:) = Vlist(4,1,:);
Vl5list(1,:) = Vlist(5,1,:);
Volist(1,:) = Vlist(7,1,:);

figure(5)
plot((1:timecuts).*dt,Volist(1,:))
xlabel('Time(s)')
ylabel('Voltage')
title('Vin and Vout of Gaussian Pulse')
hold on
plot((1:timecuts).*dt,Vl1list(1,:))
hold off

figure(6)
g = abs(fftshift(fft(Volist(1,:))));

```


```



plot(((1:length(g))/timecuts)-0.5,g)
xlim([-0.05 0.05])
xlabel('frequency')
ylabel('magnitude')
title('Fourier transform of output')



disp('Comment on what happens when time step is increased')
disp('By increasing the time step it will make the model less
    accurate.')


```

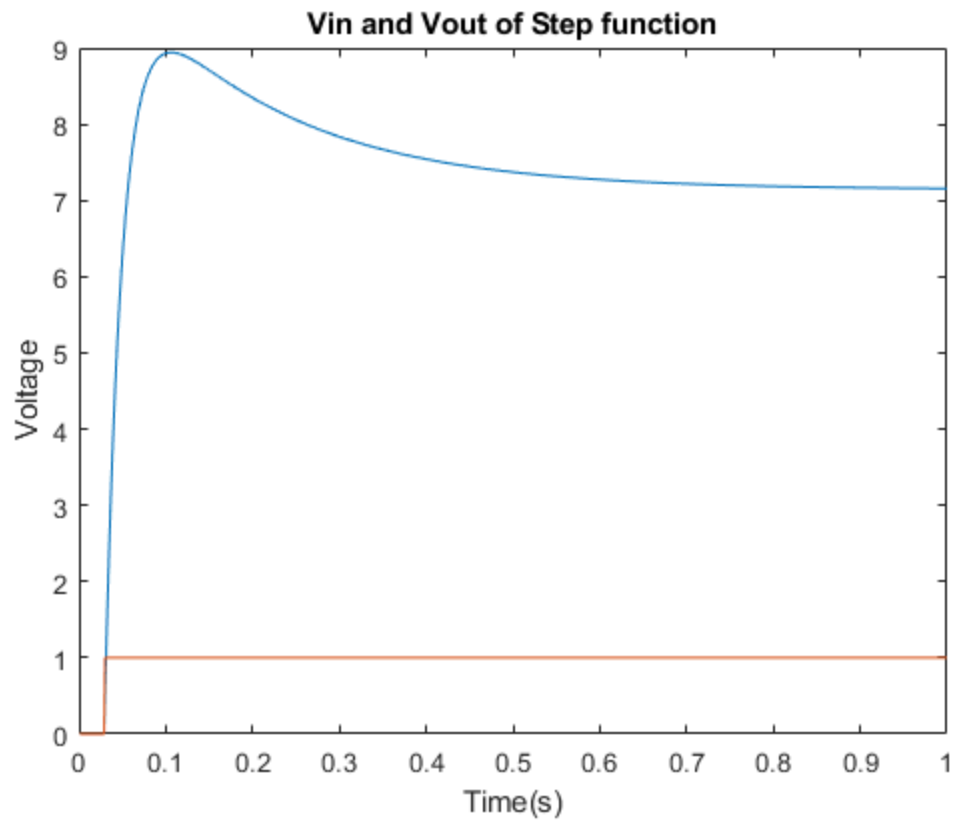A. The circuit behaves like a low pass filter
 B. I would expect that the circuit has a passband at lower frequency
 and a 2nd order drop off will happen at cut-off frequency
 Comment on what happens when time step is increased
 By increasing the time step it will make the model less accurate.



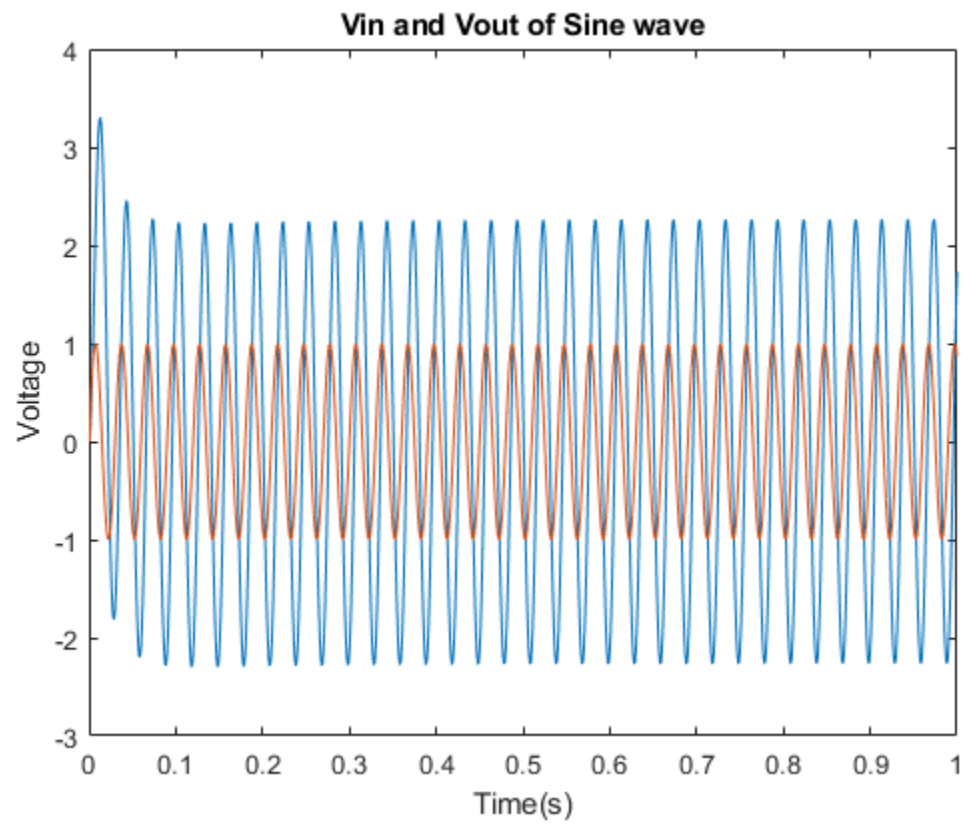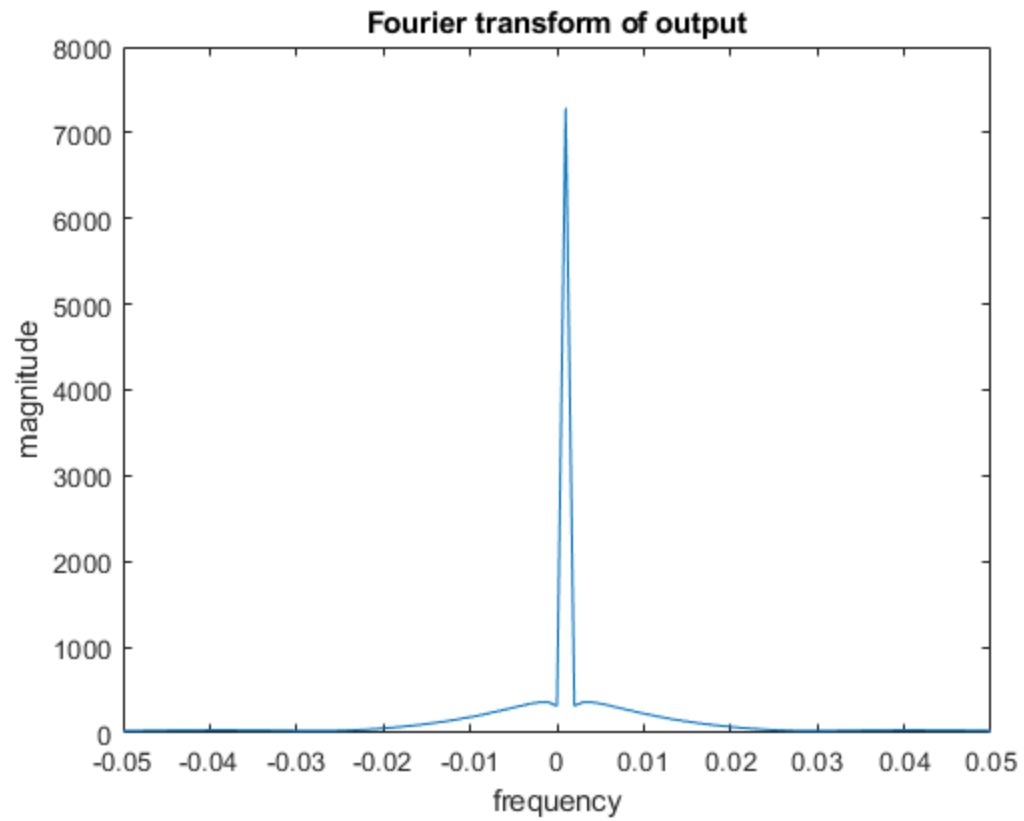

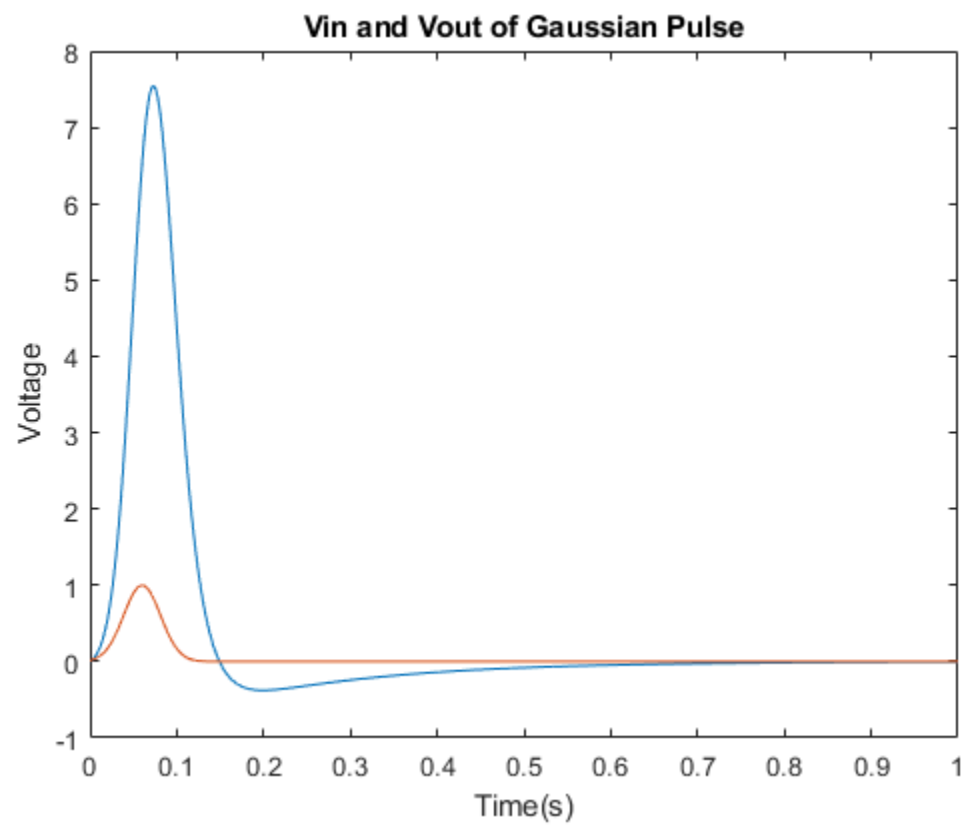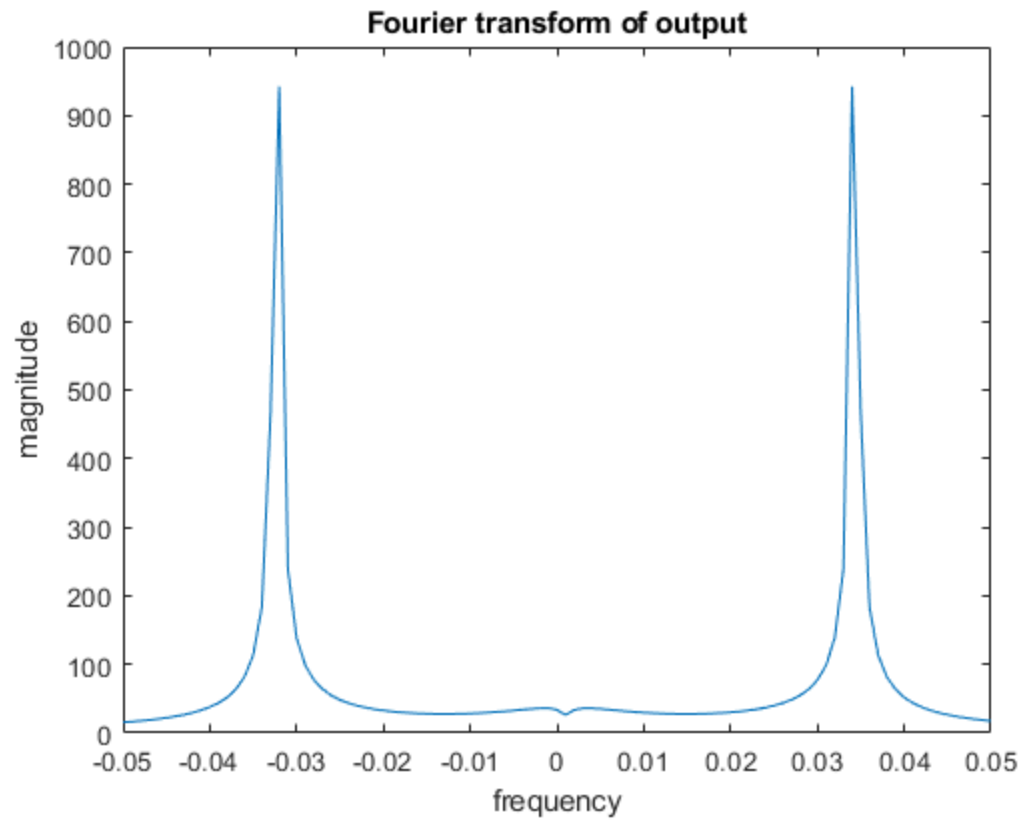

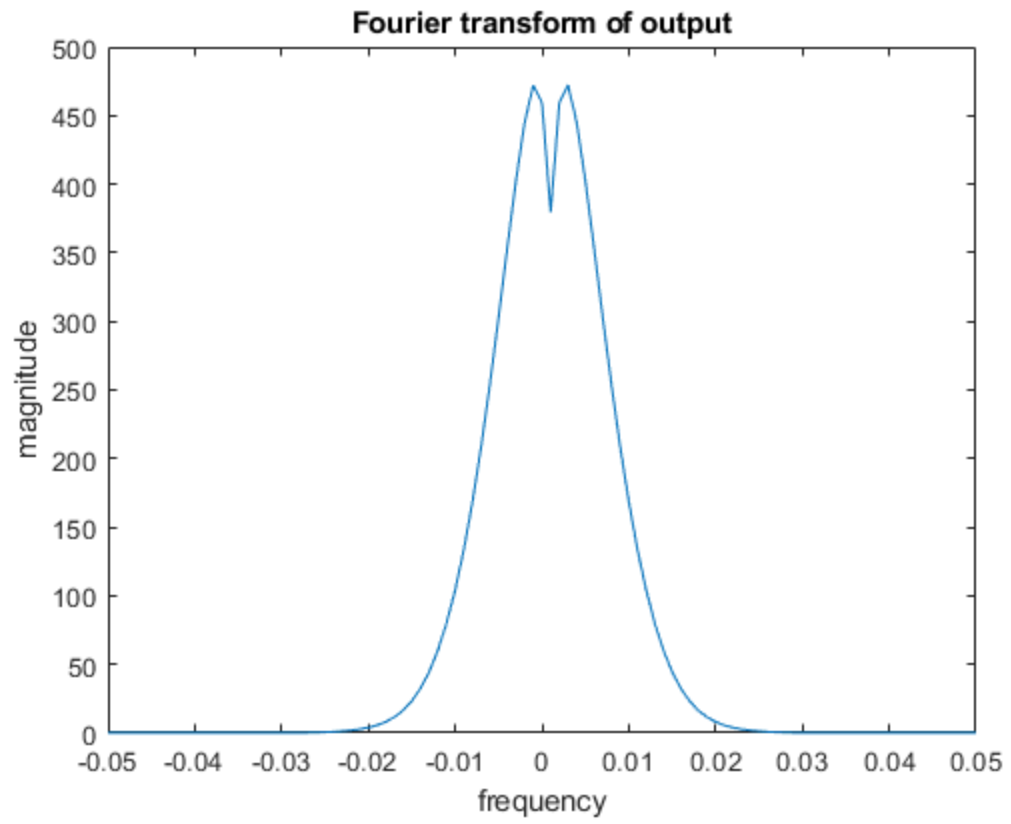

Published with MATLAB® R2018b