
```

clear all

R1=1;
C1=0.25;
R2=2;
L1=0.2;
R3=10;
a=100;
R4=0.1;
Ro=1000;

%      V1      V2      V3      V5      IL3
% G = [-1/R1, 0,      0,      0,      0; ...%N1
%      1/R1 , -1/R2, 0,      0,      0; ...%N2
%      0,      0,      -1/R3, 0,      0; ...%N3
%      0,      0,      -a/(R3*R4), -1/R4, 0; ...%N4

C = [ 0, 0, 0, 0, 0, 0, 0; ...
      -C1,C1, 0, 0, 0, 0, 0; ...
      0, 0, -L1, 0, 0, 0, 0; ...
      0, 0, 0, 0, 0, 0, 0; ...
      0, 0, 0, 0, 0, 0, 0; ...
      0, 0, 0, 0, 0, 0, 0];

G = [ 1,      0, 0, 0, 0, 0, 0; ...
      -1/R1, (1/R2 + 1/R1), -1, 0, 0, 0, 0; ...
      0,      1, 0, -1, 0, 0, 0; ...
      0,      0, -1, 1/R3, 0, 0, 0; ...
      0,      0, 0, 0, -a, 1, 0; ...
      0,      0, 0, 1/R3, -1, 0, 0; ...
      0,      0, 0, 0, 0, -1/R4, (1/R4 + 1/Ro)];

V1 = 10;
F = [V1; 0; 0; 0; 0; 0; 0];

w = 0;
V = (G+1i*w*C)\F;

for k =1:21
    vp = -10 +k -1;
    F(1,1) = vp;

    V(:, :,k) = (G+1i*w*C)\F;
end

Vo(1,:) = V(7,1,:);
V3(1,:) = V(4,1,:).*R3;

```

```
figure(1)
plot(-10:1:10,Vo)
title('DC: Vo for -10 to 10 V V1')

figure(2)
plot(-10:1:10,V3)
title('DC: V3 for -10 to 10 V V1')

%changing omega
F(1,1) =10;
for w = 1:1000
    V(:, :,w) = (G+1i*w*C)\F;
end

clear Vo
Vo(1,:) = V(7,1,:);

Vol = 20*log10(Vo/V1);

figure(3)
semilogx(1:1000,Vol)
title('AC: Gain in dB with varying w')

%Random perturbations on C's
w=pi;
std = 0.05;
for i = 1:100
    Cnew = normrnd(C1,std);
    C(2,1) = -Cnew;
    C(2,2) = Cnew;



    V(:, :,i) = (G+1i*w*C)\F;
end



clear Vo
Vo(1,:) = V(7,1,:);

Vol = 20*log10(Vo/V1);

figure(4)
hist(real(Vol(:)))
title('AC: Gain with varying C')
```

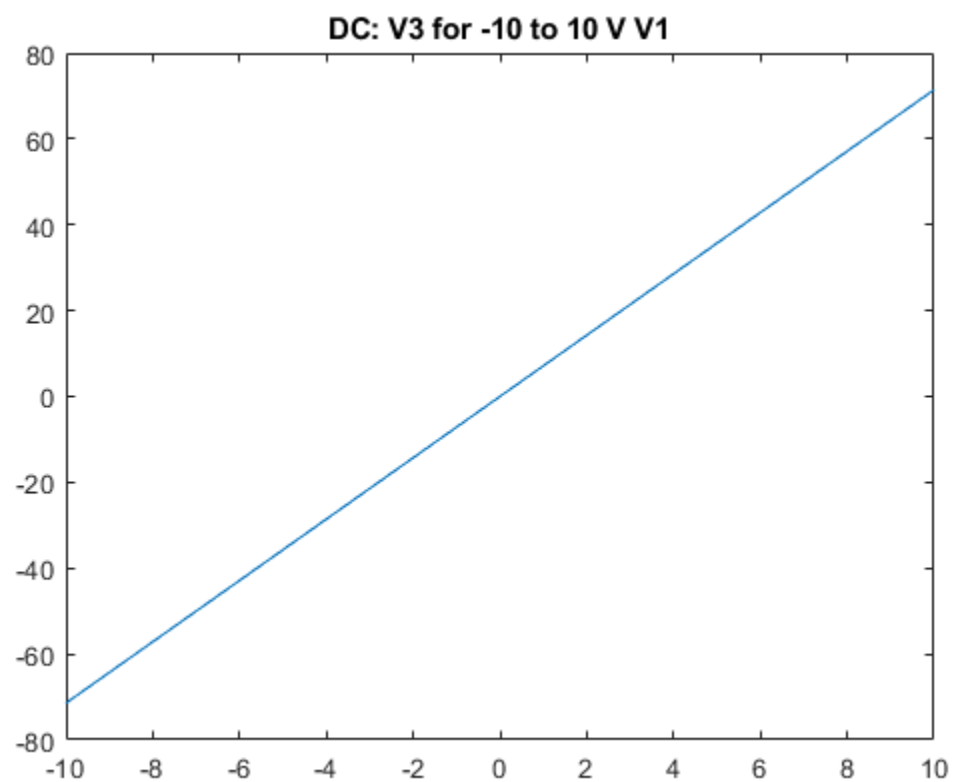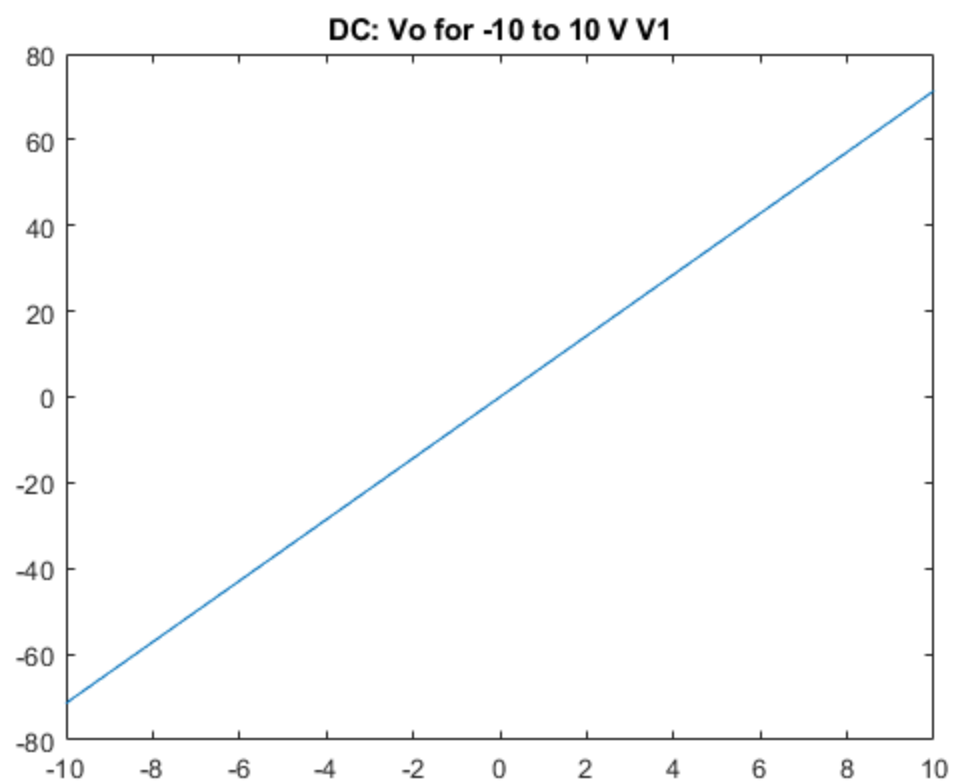Warning: Imaginary parts of complex X and/or Y arguments ignored



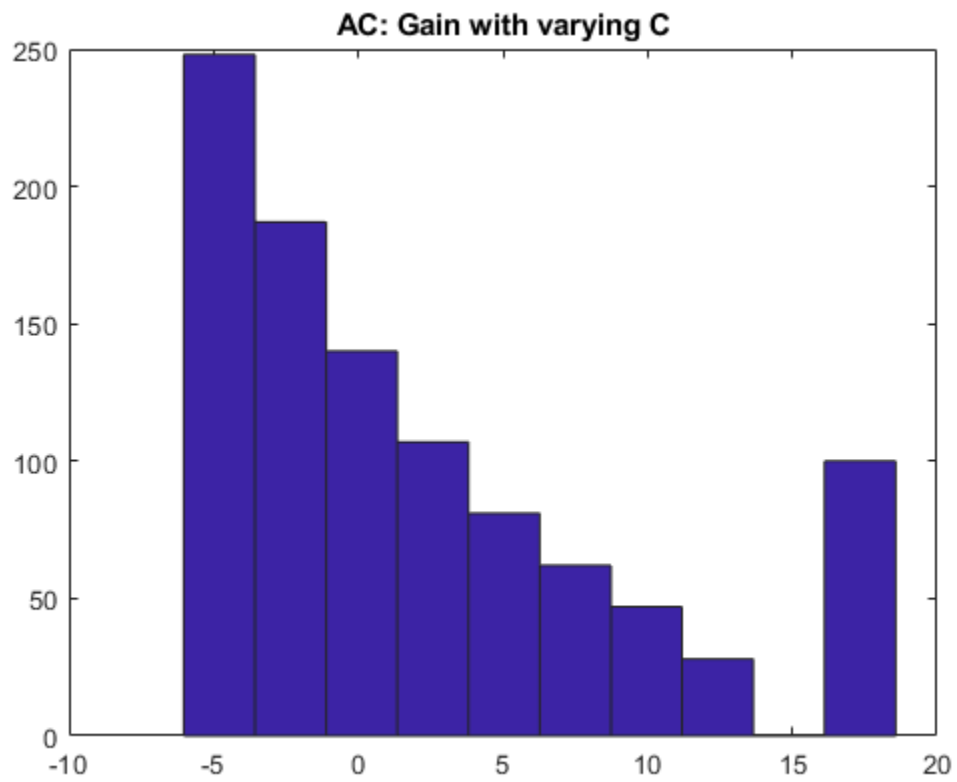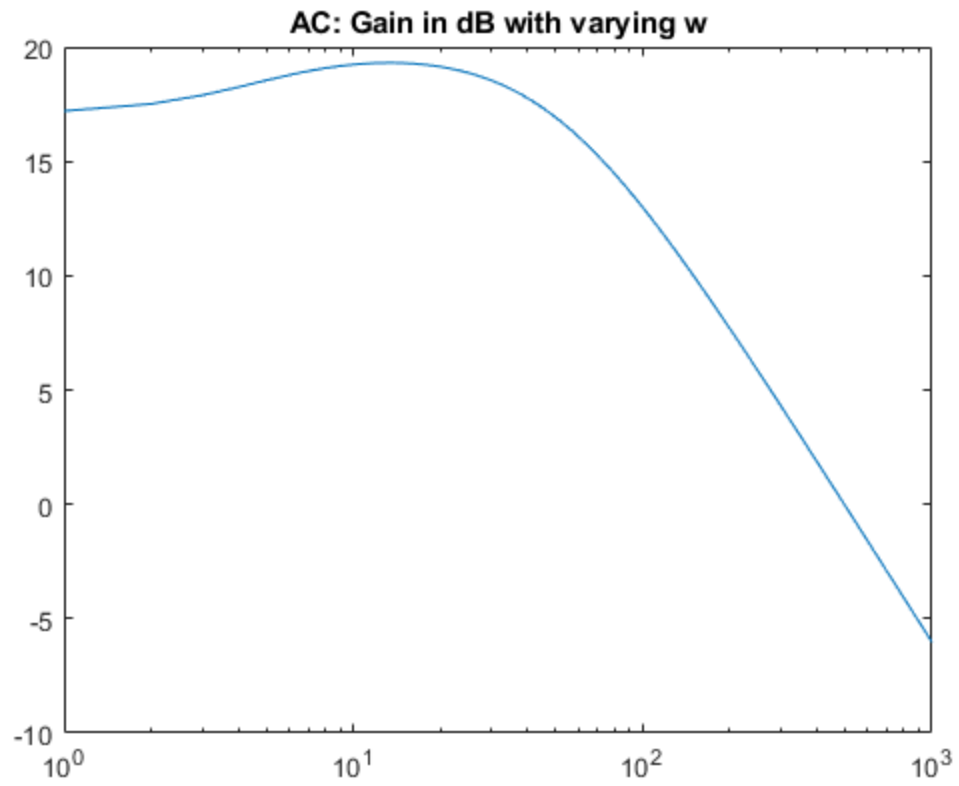

Published with MATLAB® R2018b